

# *Computer Organization*

## *Register Transfer Logic*



Department of Computer Science  
Missouri University of Science & Technology  
hurson@mst.edu


# *Computer Organization*

Note, this unit will be covered in three lectures. In case you finish it earlier, then you have the following options:

- 1) Take the early test and start CS3889.module3
- 2) Study the supplement module (supplement CS3889.module2)
- 3) Act as a helper to help other students in studying CS3889.module2

Note, options 2 and 3 have extra credits as noted in course outline.

# Computer Organization

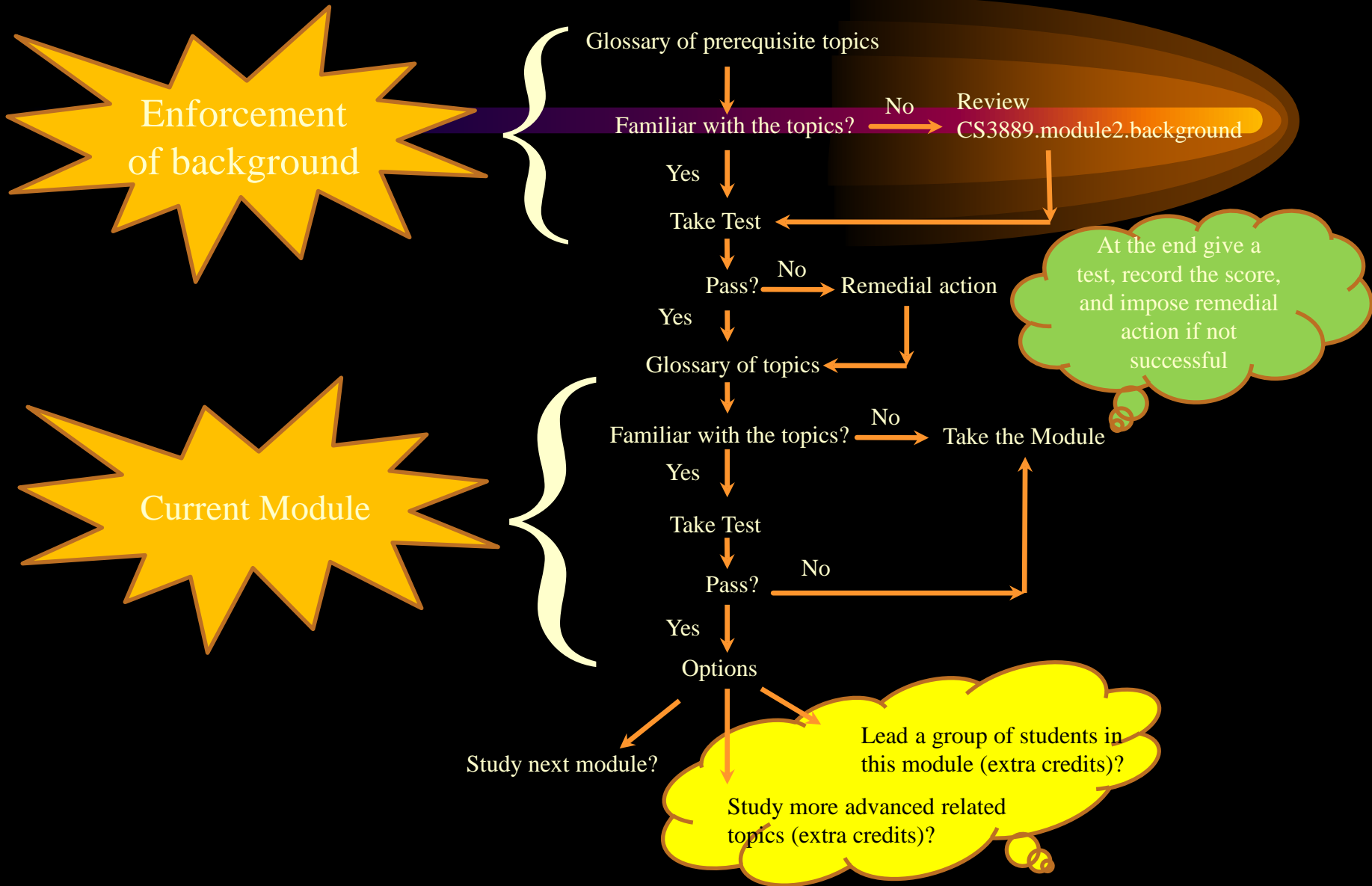

# *Computer Organization*

## ◆ Register Transfer Language (RTL)

★ Like any other language, the RTL is:

- A set of symbols and rules to describe:
  - Elementary objects,
  - Syntax, and
  - Semantics of the system.
- Composed of two parts:
  - Declaration Part
  - Execution Part

# *Computer Organization*

## ◆ Register Transfer Language (RTL)

★ **Declaration Part** is used to describe the basic components (elementary objects):

- A Set of registers and their functions.
- The binary coded information in the registers.
- The operations performed on the information stored in the registers.
- The control functions that initiate the sequence of the operations.

# Computer Organization

## ◆ Register Transfer Language (RTL)

★ **Execution part** is a collection of statements. Each statement is composed of two parts:

- **Control Part (label):** is a Boolean function, which determines under what condition the corresponding operation (s) is (are) going to be executed.
- **Operational Part:** determines the data manipulation actions ( $\mu$ -operation).

$T_1: A \leftarrow (B)$

$T_2: A \leftarrow (A)+(B)$

Control Part

Operational part

# *Computer Organization*

## ◆ Register Transfer Language:

★ There is a one-to-one relationship between the components in RTL and our earlier view at the computer:

- Set of registers  $\equiv$  memory system
- $\mu$ -operations  $\equiv$  ALU
- Control functions  $\equiv$  CU

# Computer Organization

## ◆ Register Transfer Language:

★ **Register**: It is a group of binary cells suitable for holding binary information. In RTL notation it is represented by Capital letters:

**MAR, A, B, IR, ...**

★ Bits in a register are numbered - either from left-to-right or right-to-left, starting either from 0 or 1.

Declare Register                    **A(8), MBR(12), PC(16), ...**

Declare Sub-Register                **PC(L)=PC(1-8), PC(H)=PC(9-16)**



# *Computer Organization*

## ◆ Register Transfer Language:

★ Memory can be viewed as a 2-dimensional storage medium:

Declare Memory M[0:5, 0:15]

# Computer Organization

## ◆ Register Transfer Language: Register

★ Storage media (registers) can be classified based on various parameters:

### ★ Access Time

- Fast access storage ("register")
  - General purpose register (R1-R16 in IBM)
  - Special purpose register (PC,IR, ...)
- Slower access storage (main memory)


### ★ Functionality

- Storage type ( $R_1$ - $R_{16}$  in IBM)
- Operational type (AC, PC)

# Computer Organization
 
## ◆ Register Transfer Language: Register

★ Graphically a register is represented by a rectangle:



# Computer Organization


## ◆ Register Transfer Language: Operations

- ★ A  $\mu$ -operation is an elementary operation which is executed in one clock pulse period.
- ★ Four classes of  $\mu$  -operations will be discussed:
  - Inter-register Transfer,
  - Arithmetic,
  - Logic, and
  - Shift

# Computer Organization
 
## ◆ Register Transfer Language: Inter-register Transfer

- ★ It is this class of operations which allows data to be transferred from one storage unit to another.



# Computer Organization

## ◆ Register Transfer Language: Inter-register Transfer

★ It can be divided into two groups:

- Register Transfer and
- Memory Transfer

★ Inter-register transfer operations can be performed in two fashions:

- **Serial:** During each clock pulse one bit of source is transferred to the destination.
- **Parallel:** During a clock pulse the whole contents of source is transferred to the destination.

# Computer Organization

## ◆ Register Transfer Language: Inter-register Transfer

- ★ **Register Transfer:** is the class of operations that determines the data transfer between "registers".
- ★ **Memory Transfer:** is the class of operations that determines how data stored in memory can be accessed.
- ★ Note: i) Conventional main memory is random access memory. ii) Any access to main memory is through **Memory Address Register (MAR)** and **Memory Buffer Register (MBR)**. Two major operations can be recognized: **READ, WRITE**.

# Computer Organization

## ◆ Register Transfer Language: Memory Transfer

### ★ Read

$R_1:$  MAR  $\leftarrow$  "address"

$R_2:$  MBR  $\leftarrow$  (M[MAR])

### ★ Write

$W_1:$  MAR  $\leftarrow$  "address"

$W_2:$  MBR  $\leftarrow$  "data"

$W_3:$  M[MAR]  $\leftarrow$  (MBR)



# *Computer Organization*

## ◆ Question

- ★ What is the minimum number of operations which allows all possible arithmetic operations?
- ★ What are they?
- ★ What is the minimum number of operations which allows all possible logic operations?
- ★ What are they?

# Computer Organization

## ◆ Register Transfer Language: Arithmetic Operations

★ Two basic operations will be studied: **ADD** and **Complement**.

$$T_1: F \leftarrow (A) + (B)$$

$$T_1: A \leftarrow (\overline{A})$$

$$T_1: A \leftarrow (\tilde{A}) \quad \text{Note: } (\tilde{A}) = (\overline{A}) + 1$$

# Computer Organization

## ◆ Register Transfer Language: Arithmetic Operations

★ Subtraction, Multiplication, and Division can be performed directly; or,

$$T_1: F \leftarrow (A) - (B) \quad T_{11}: F \leftarrow (\overline{B}) + 1$$

$$T_{12}: F \leftarrow (A) + (F)$$

$$T_1: F \leftarrow (A) * (B) \quad \text{repeated additions}$$

$$T_1: F \leftarrow (A) / (B) \quad \text{repeated subtractions}$$

# Computer Organization


## ◆ Register Transfer Language: Addition

★ Basic building blocks:

● Half adder (H. A.)

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = A \wedge B$$

 


# Computer Organization

## ◆ Register Transfer Language: Half Adder

### Truth Table

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

### Realization

 

**Timing:** If  $\Delta t$  is the delay time of a basic logic gate (OR, AND), then the delay of Half Adder =  $2 \Delta t$ .

# Computer Organization


## ◆ Register Transfer Language: Addition

★ Basic building blocks:

● Full Adder (F.A.)

$$\text{Sum} = A \oplus B \oplus \text{Carry-in}$$
 
$$\text{Carry-out} = A \wedge B + (A \oplus B) \wedge \text{Carry-in}$$




# Computer Organization

## ◆ Register Transfer Language: Full Adder

### Truth Table

A	B	Carry-in	Sum	Carry-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

### Realization

 


★ **Timing:** If  $\Delta t$  is the delay time of a basic logic gate (OR, AND), then the delay of Full Adder =  $4\Delta t$ .

# Computer Organization

## ◆ Register Transfer Language: Serial Adder

- ★  $R_1$  and  $R_2$  are circular shift registers.
- ★  $R_3$  is a shift register.

$$R_3 \leftarrow (R_1) + (R_2)$$

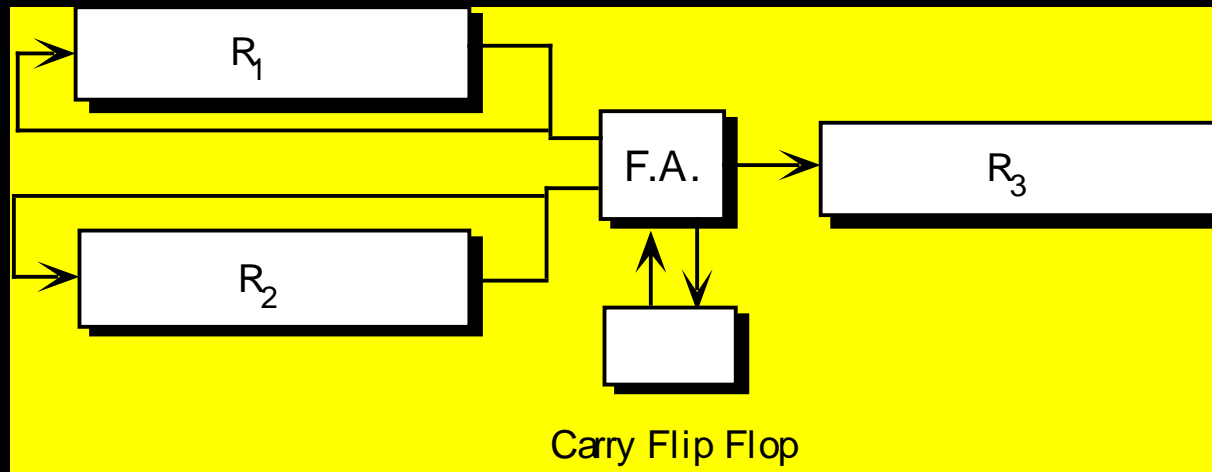




# Computer Organization

## ◆ Register Transfer Language: Parallel Adder

★ A cascade of  $n$  full adders.

$$R_3 \leftarrow (R_1) + (R_2)$$

 

# *Computer Organization*



## ◆ Question


- ★ Parallel operations are faster and more expensive than serial operations.
- ★ What are the Delay times of serial and parallel adders?
- ★ How to improve the performance of parallel adder?

# *Computer Organization*

- ◆ **Register Transfer Language:  $2^s$  Complement**
  - ★ A simple combinational circuit can be developed to perform  $2^s$  complement operation.
  - ★ Assuming T type Flip Flops, when activation signal (P) is high the following circuit performs  $2^s$  complement operation.

# Computer Organization
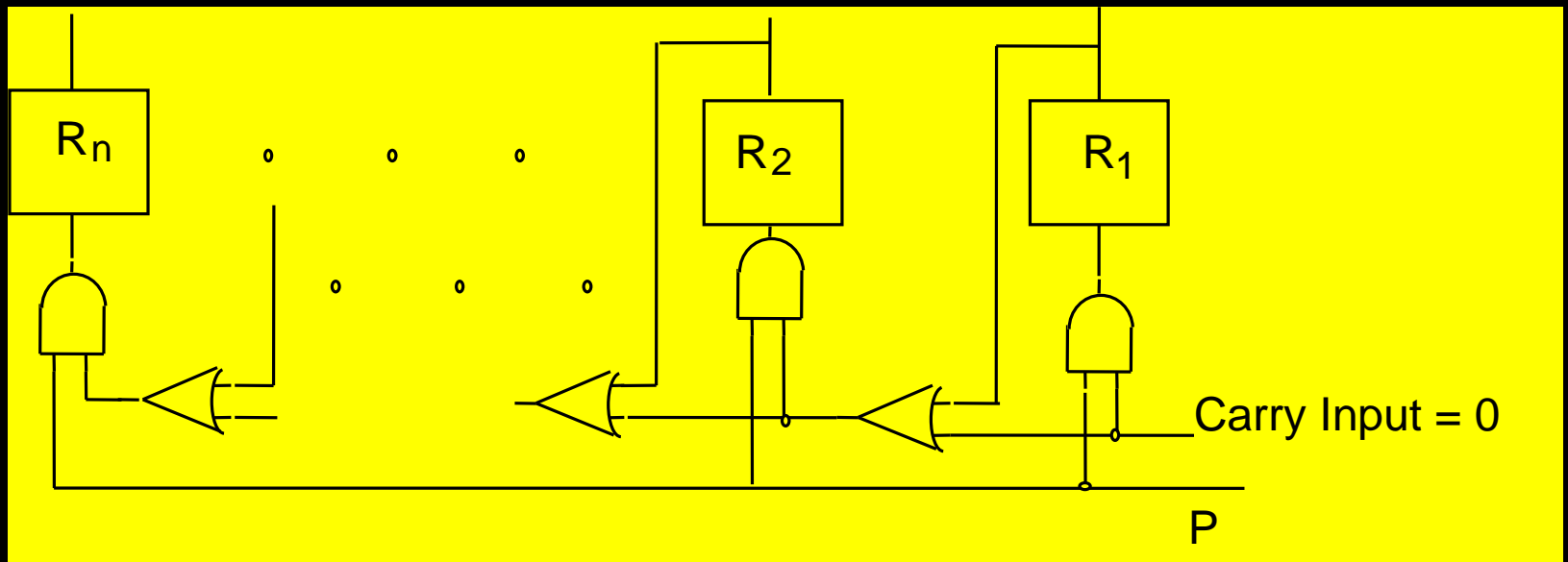
## ◆ Register Transfer Language: $2^s$ Complement



# *Computer Organization*

## ◆ Question

- ★ How is the value of  $P$  determined?
- ★ Modify the  $2^s$  complement circuit for  $1^s$  complement operation.

# *Computer Organization*

- ◆ **Register Transfer Language: Logic Operations**
  - ★ With two binary bits one can have up to sixteen different logic operations.
  - ★ One needs to have either (AND, NOT) or (OR, NOT) combination in order to implement all possible logic operations.

# Computer Organization

## ◆ Register Transfer Language: Logic Operations

- ★ Logic operations can be used in order to implement other functions.
- ★ Logic operations are useful in string and pattern matching operations.

$$T_1 : A \leftarrow (A) \wedge (B)$$

$$T_2 : A \leftarrow (A) \oplus (B)$$

# Computer Organization

## ◆ Register Transfer Language: Logic Operations

★ **selective set** — Set the bits in register A where there are corresponding 1s in register B.

$$A = 1001$$

$$B = 1011$$

$$A \leftarrow A \cup B = 1011$$

★ **selective complement** — Complement bits in A where there are corresponding 1s in B.

$$A = 1001$$

$$B = 1010$$

$$A \leftarrow A \oplus B = 0011$$



# Computer Organization

## ◆ Register Transfer Language: Logic Operations

- ★ Transfer operation can be performed by logic operations.

$$A = 1001$$

$$B \leftarrow 0000$$

$$B = 1100$$

$$B \leftarrow A \cup B = 1001$$

- ★ Contents of two registers can be compared against each other by logic operation.

$$A = 1010$$

$$A \text{ XOR } B = 0000$$

$$B = 1010$$

$$A \text{ XNOR } B = 1111$$

# *Computer Organization*

- ◆ **Register Transfer Language:** Shift Operations
  - ★ Shift operations can be used to perform transfer as well as arithmetic operations.
  - ★ To accomplish such an operation, one has to specify two parameters:
    - Direction - i.e., Left or Right
    - Number of positions

# *Computer Organization*

## ◆ **Register Transfer Language: Shift Operations**

★ Four types of shift operations can be distinguished:

- Serial Shift
- Circular Shift
- Logical Shift
- Arithmetic Shift

# Computer Organization


## ◆ Questions

- \* Parallel is faster than Serial?
- \* Parallel is more expensive than Serial?
- \* How to transfer data among "registers"?
  - Direct Transfer?
  - Busing Technique?
- \* Compare and contrast **direct transfer** against **busing technique**.
- \* What is the difference between RAM, DAM, and SAM?
- \* What determines the length of MAR and MBR?
- \* How are the lengths of MAR and MBR determined?


# Computer Organization
 
## ◆ Register Transfer Language: Shift Operations

- ★ In **serial shift** the extreme bit, left-most or right-most, will receive its contents from outside:



 
- ★ In **circular shift** one extreme bit assumes the contents of the other:



# Computer Organization
 
## ◆ Register Transfer Language: Shift Operations

- ★ In **logical shift** the extreme bit, depending on the direction, always assumes the value 0:



# Computer Organization

## ◆ Register Transfer Language: Shift Operations

- ★ In **arithmetic shift** the contents of the register is assumed to be a signed number.
- ★ In **arithmetic shift**:
  - Sign should be preserved
  - Shift right should divide the contents by 2
  - Shift left should multiply the contents by 2
- ★ To satisfy the above conditions one has to develop different routines based on the representation of the number - i.e., **signed magnitude**, **signed 1<sup>s</sup> complement**, and **signed 2<sup>s</sup> complement**.

# Computer Organization

## ◆ Register Transfer Language: Arithmetic Shift

Data representation	Sign bit	Procedure
Positive	Unchanged	Added bit is zero
Negative Signed Mag.	Unchanged	Added bit is zero
Negative 1 <sup>s</sup> Complement	Unchanged	Added bit is one
Negative 2 <sup>s</sup> Complement	Unchanged	Added bit is zero (Shift left)
Negative 2 <sup>s</sup> Complement	Unchanged	Added bit is one (Shift right)



# Computer Organization

## ◆ Register Transfer Language: Arithmetic Shift

### ★ Signed magnitude number

- Perform logical shift on the magnitude part.
- Do not change the sign bit.

### ★ $1^s$ complement and $2^s$ complement number:

- The whole number should be operated on.
- For  $1^s$  complement duplicate the sign bit for extreme bit.
- For  $2^s$  complement shift right duplicate the sign bit.
- For  $2^s$  complement shift left perform the logic shift.

# Computer Organization

## ◆ Register Transfer Language: Arithmetic Shift (Example)

★ Assume

A =

0 0 1 0 1

B =

1 1 0 1 0

★ Signed magnitude

● AShift A Left

0 1 0 1 0

AShift B Right

1 0 1 0 1

# Computer Organization

## ◆ Register Transfer Language: Arithmetic Shift (Example)

### ★ 1<sup>s</sup> Complement

● AShift A Right

0 0 0 1 0

AShift B Right

1 1 1 0 1

AShift B Left

1 0 1 0 1

# Computer Organization

## ◆ Register Transfer Language: Arithmetic Shift (Example)

★  $2^s$  complement

● AShift B Right

1 1 1 0 1

AShift B Left

1 0 1 0 0

★ Assume C = 1 0 1 1 0 is in  $2^s$  complement.

AShift C Left => 0 1 1 0 0

Signed has not been preserved! Why?

# *Computer Organization*

## ◆ Register Transfer Language

- ★ **Full adder:** A basic building block for the design of an adder. It can be designed as a cascade of two half adders.
- ★ **Half adder:** A basic building block — a combinational logic — for the design of an adder. It accepts two binary bits and generates the sum and carry.
- ★ **micro operation:** A basic operation that can be executed during a single clock pulse.

# Computer Organization

## ◆ Register Transfer Language

- ★ **Parallel adder:** A way to add two binary numbers — addition will be initiated simultaneously on all of the operand bit pairs.
- ★ **Serial adder:** A way to perform addition. During each clock pulse one pair of the operand bits will participate in the operation.
- ★ **Overflow:** Inability to store a number in its entirety in a register.
- ★ **Interregister transfer operation:** A class of micro operations that allows data transfer between a source and destination registers.

# Computer Organization

## ◆ Questions

- ★ **True or false:** in general, read from memory is faster than writing into the memory!
- ★ **Assume** that  $\Delta t$  is the delay of a simple logic gate — i.e., an AND or OR gate, what is the execution time of an n-bit parallel adder?
- ★ **True or false:** parallel operation is faster than serial operation (justify)!

# Computer Organization

## ◆ Questions

- ★ **True or false:** one needs more hardware support for parallel operations than serial operations!
- ★ **Write** a simple software program to perform multiplication as a sequence of additions.
- ★ **Write** a simple software program to perform division as a sequence of subtractions.
- ★ **How** can we use the same combinational logic for the  $2^s$  complement operation to perform the  $1^s$  complement operation?



# Computer Organization

## ◆ Questions

- ★ **Equality** between two binary bit patterns can be determined by using exclusive OR operation. Do you know any other logic operation to carry out the same operation?
- ★ **If  $\Delta t$**  is the delay of a simple logic gate — i.e., an AND or OR gate, then what is the execution time of a parallel AND operation, and what is the execution time of a serial AND operation?