 


Computer Organization
Arithmetic Logic Unit
Background



Department of Computer Science
Missouri University of Science & Technology
hurson@mst.edu



X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Truth Table for a combinational logic



X	Y	X AND Y
0	0	0
0	1	0
1	0	0
1	1	1



X	Y	X OR Y
0	0	0
0	1	1
1	0	1
1	1	1




X	NOT X
0	1
1	0

Basic logic elements: (a) AND; (b) OR; (c) NOT (inverter).




X	Y	X NAND Y
0	0	1
0	1	1
1	0	1
1	1	0

 

X	Y	X NOR Y
0	0	1
0	1	0
1	0	0
1	1	0

Inverting gates: a) NAND, b) NOR

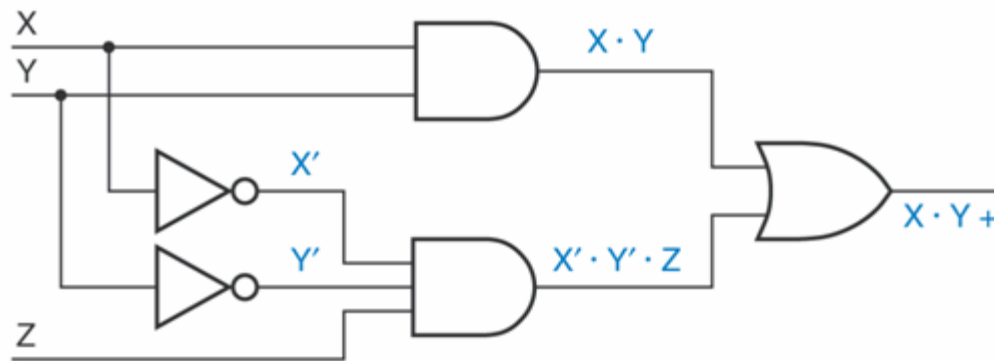

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


A combinational circuit with its truth table

(T1)	$X + 0 = X$	(T1')	$X \cdot 1 = X$	(Identities)
(T2)	$X + 1 = 1$	(T2')	$X \cdot 0 = 0$	(Null elements)
(T3)	$X + X = X$	(T3')	$X \cdot X = X$	(Idempotency)
(T4)	$(X')' = X$			(Involution)
(T5)	$X + X' = 1$	(T5')	$X \cdot X' = 0$	(Complements)

Switching algebra theorems with one variable

(T6)	$X + Y = Y + X$	(T6')	$X \cdot Y = Y \cdot X$	(Commutativity)
(T7)	$(X + Y) + Z = X + (Y + Z)$	(T7')	$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$	(Associativity)
(T8)	$X \cdot Y + X \cdot Z = X \cdot (Y + Z)$	(T8')	$(X + Y) \cdot (X + Z) = X + Y \cdot Z$	(Distributivity)
(T9)	$X + X \cdot Y = X$	(T9')	$X \cdot (X + Y) = X$	(Covering)
(T10)	$X \cdot Y + X \cdot Y' = X$	(T10')	$(X + Y) \cdot (X + Y') = X$	(Combining)
(T11)	$X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$			(Consensus)
(T11')	$(X + Y) \cdot (X' + Z) \cdot (Y + Z) = (X + Y) \cdot (X' + Z)$			

Switching algebra theorems with two or three variables variable



(T12)	$X + X + \dots + X = X$	(Generalized idempotency)
(T12')	$X \cdot X \cdot \dots \cdot X = X$	
(T13)	$(X_1 \cdot X_2 \cdot \dots \cdot X_n)' = X_1' + X_2' + \dots + X_n'$	(DeMorgan's theorems)
(T13')	$(X_1 + X_2 + \dots + X_n)' = X_1' \cdot X_2' \cdot \dots \cdot X_n'$	
(T14)	$[F(X_1, X_2, \dots, X_n, +, \cdot)]' = F(X_1', X_2', \dots, X_n', \cdot, +)$	(Generalized DeMorgan's theorem)
(T15)	$F(X_1, X_2, \dots, X_n) = X_1 \cdot F(1, X_2, \dots, X_n) + X_1' \cdot F(0, X_2, \dots, X_n)$	(Shannon's expansion theorems)
(T15')	$F(X_1, X_2, \dots, X_n) = [X_1 + F(0, X_2, \dots, X_n)] \cdot [X_1' + F(1, X_2, \dots, X_n)]$	


Switching-algebra theorems with n variables.

Generalized DeMorgan's theorem


- ◆ The complement of a logic expression F , which is denoted as $(F)'$, is an expression whose value is the opposite of F 's for every possible input combination.
- ◆ T14 states that given any n -variable logic expression, its complement can be obtained by swapping $+$ and $.$ and complementing all variables.
- ◆ Example:

$$\begin{aligned} * F(W,X,Y,Z) &= (W'.X) + (X.Y) + (W.(X'+Z')) \\ &= ((W)'.X) + (X.Y) + (W.((X)'+(Z)')) \end{aligned}$$
 
$$\begin{aligned} * [F(W,X,Y,Z)]' &= (((W)')'+X') . (X'+Y') . (W'+(((X)')'.((Z)')')) \\ &= (W+X') . (X'+Y') . (W'+(X.Z)) \end{aligned}$$



 Equivalent circuits according to DeMorgan's theorem T13: (a) AND-NOT; (b) NOT-OR; (c) logic symbol for a NAND gate; (d) equivalent symbol for a NAND gate.



Equivalent circuits according to DeMorgan's theorem T13': (a) OR-NOT; (b) NOT-AND; (c) logic symbol for a NOR gate; (d) equivalent symbol for a NOR gate.

Principle of duality

- ◆ Any theorem or identity in switching algebra remains true if 0 and 1 are swapped and \cdot and $+$ are swapped throughout.
- ◆ If $F(X_1, X_2, \dots, X_n)$ is a fully parenthesized logic expression involving the variables X_1, X_2, \dots, X_n and the operators $\cdot, +$, and $'$, then the dual of F , denoted as F^D , is the same expression with $+$ and \cdot swapped.
- ◆ $F^D(X_1, X_2, \dots, X_n, +, \cdot, ') = F(X_1, X_2, \dots, X_n, \cdot, +, ')$
- ◆ Generalized DeMorgan's theorem can be restated as:
 - ★ $[F(X_1, X_2, \dots, X_n)]' = F^D(X'_1, X'_2, \dots, X'_n)$

Row	X	Y	Z	F
0	0	0	0	F(0,0,0)
1	0	0	1	F(0,0,1)
2	0	1	0	F(0,1,0)
3	0	1	1	F(0,1,1)
4	1	0	0	F(1,0,0)
5	1	0	1	F(1,0,1)
6	1	1	0	F(1,1,0)
7	1	1	1	F(1,1,1)

Table 4-4

General truth table structure for a 3-variable logic function, F(X,Y, Z).

$$F = \sum_{X,Y,Z}(0,3,4,6,7)$$

$$F = \prod_{X,Y,Z}(1,2,5)$$

Row	X	Y	Z	F
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

Table 4-5

Truth table for a particular 3-variable logic function, F(X,Y, Z)

Definitions

- ◆ A *literal* is a variable or the complement of a variable.
 - ✱ Examples: X , Y , X' , Y'
- ◆ A *product term* is a single literal or a logical product of two or more literals.
 - ✱ Examples: Z' , $W.X.Y$, $X.Y'.Z$
- ◆ A *sum-of-products (SOP) expression* is a logical sum of product terms.
 - ✱ Example: $Z' + W.X.Y + X.Y'.Z$
- ◆ A *sum term* is a single literal or a logical sum of two or more literals.
 - ✱ Examples: Z' , $W+X+Y$, $X+Y'+Z$
- ◆ A *product-of-sums (POS) expression* is a logical product of sum terms.
 - ✱ Example: $Z'.(W+X+Y).(X+Y'+Z)$

More definitions

- ◆ A *normal term* is a product or sum term in which no variable appears more than once.
 - ★ A nonnormal term can always be simplified to a constant or a normal term using one of theorems T3, T3', T5, or T5'.
 - ★ Examples of nonnormal terms:
 $W.X.X'.Y$, $W+W+X'+Y$
 - ★ Examples of normal terms: $W.X.Y'$, $W+X'+Y$
- ◆ An *n-variable minterm* is a normal product term with n literals. There are 2^n such product terms.
 - ★ Some examples of 4-variable minterms:
 $W'.X'.Y'.Z'$, $W.X.Y'.Z$
 - ★ A minterm can be defined as a product term that is 1 in exactly one row of the truth table.
- ◆ An *n-variable maxterm* is a normal sum term with n literals. There are 2^n such sum terms.
 - ★ Some examples of 4-variable maxterms:
 $W'+X'+Y'+Z'$, $W+X+Y'+Z$
 - ★ A maxterm can be defined as a sum term that is 0 in exactly one row of the truth table.

Row	X	Y	Z	F	Minterm	Maxterm
0	0	0	0	F(0,0,0)	$X' \cdot Y' \cdot Z'$	$X + Y + Z$
1	0	0	1	F(0,0,1)	$X' \cdot Y' \cdot Z$	$X + Y + Z'$
2	0	1	0	F(0,1,0)	$X' \cdot Y \cdot Z'$	$X + Y' + Z$
3	0	1	1	F(0,1,1)	$X' \cdot Y \cdot Z$	$X + Y' + Z'$
4	1	0	0	F(1,0,0)	$X \cdot Y' \cdot Z'$	$X' + Y + Z$
5	1	0	1	F(1,0,1)	$X \cdot Y' \cdot Z$	$X' + Y + Z'$
6	1	1	0	F(1,1,0)	$X \cdot Y \cdot Z'$	$X' + Y' + Z$
7	1	1	1	F(1,1,1)	$X \cdot Y \cdot Z$	$X' + Y' + Z'$

Table 4-6

Minterms and maxterms for a 3-variable logic function, F(X,Y,Z).

Integer representation

- ◆ A minterm can be represented by an n -bit integer, the *minterm number*.
- ◆ Minterm i denotes the minterm corresponding to row i of the truth table.
 - ★ Row 5: 101 ; Minterm 5 = $X.Y'.Z$
- ◆ Opposite is true for maxterms
 - ★ Maxterm 5 = $X'+Y+Z'$

Canonical sum and product

- ◆ The *canonical sum* of a logic function is a **sum** of the **minterms** corresponding to truth table rows (input combinations) for which the function produces a **1 output**.

$$* F = \sum_{X,Y,Z}(0,3,4,6,7)$$

$$= X'.Y'.Z' + X'.Y.Z + X.Y'.Z' + X.Y.Z' + X.Y.Z$$

- ◆ The minterm list is also known as the *on-set* for the logic function. Each minterm “turns on” the output for exactly one input combination.
- ◆ Any logic function can be written as a canonical sum.
- ◆ The *canonical product* of a logic function is a **product** of the **maxterms** corresponding to truth table rows (input combinations) for which the function produces a **0 output**.

$$* F = \Pi_{X,Y,Z}(1,2,5)$$

$$= (X+Y+Z') . (X+Y'+Z) . (X'+Y+Z')$$

- ◆ The maxterm list is also known as the *off-set* for the logic function. Each minterm “turns off” the output for exactly one input combination.
- ◆ Any logic function can be written as a canonical product.

Converting between minterm and maxterm lists

- ◆ For a function of n variables, the possible minterm and maxterm numbers are between 0 and 2^n-1 .
- ◆ A minterm or maxterm list contains a subset of these numbers.
- ◆ To switch between list types, take the set complement.
- ◆ Examples:

$$\sum_{X,Y,Z}(0,1,2,3) = \Pi_{X,Y,Z}(4,5,6,7)$$

$$\sum_{X,Y}(1) = \Pi_{X,Y}(0,2,3)$$

$$\sum_{W,X,Y,Z}(0,1,2,3,5,7,11,13) = \Pi_{W,X,Y,Z}(4,6,8,9,10,12,14,15)$$

Equivalent representations for a combinational logic function

- ◆ Truth table
- ◆ Algebraic sum of minterms, the canonical sum
- ◆ A minterm using Σ notation
- ◆ Algebraic product of maxterms, the canonical product
- ◆ A maxterm using Π notation
- ◆ All of these representations provide exactly the same information as the others
- ◆ Given any one representation, the other four can be derived simply

Combinational circuit analysis

- ◆ In analyzing a logic circuit, you find a formal description of its logic function.
- ◆ Once you have that, you can represent it in all the different ways you have learned, and play with equivalent representations
- ◆ Can also feed it to a program that will generate the standard form circuit for you
 - ★ This will not necessarily be the most efficient circuit that carries out the function
 - ★ Programs are dumb

Exhaustive search

- ◆ Given an n -input circuit, construct the truth table. This involves finding the output generated for each of the 2^n possible combinations of input variables
- ◆ This will blow up for anything other than very small n
- ◆ Need a better way
- ◆ Already have it: algebraic representation
 - ★ Use variable names rather than explicit values

Exhaustive search

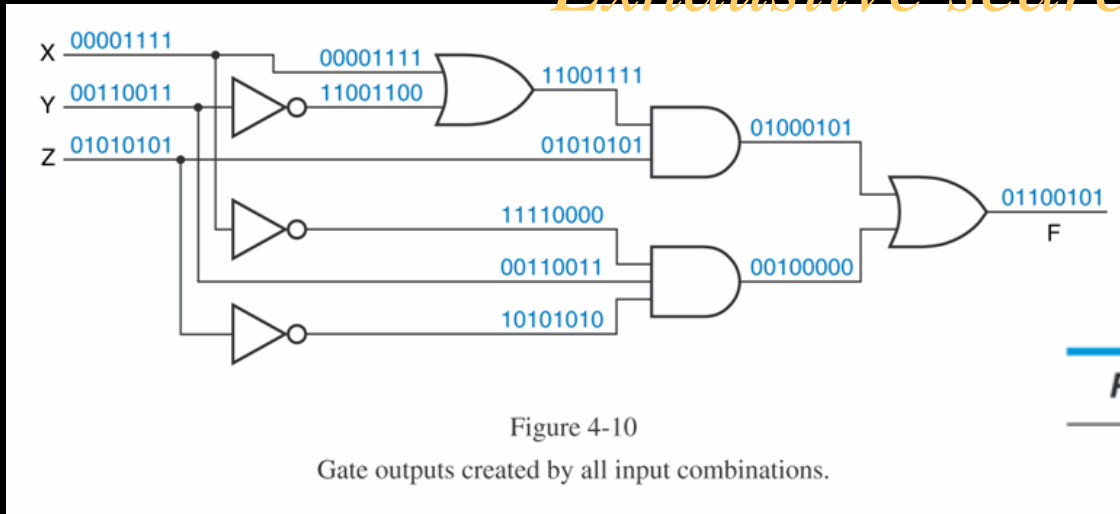


Figure 4-10
Gate outputs created by all input combinations.

Row	X	Y	Z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1

Table 4-7

Truth table for the logic circuit of Figure 4-9.

Algebraic representation

 


Figure 4-11

Logic expressions for signal lines

Equivalent circuit

$$\begin{aligned} \blacklozenge F &= ((X+Y') \cdot Z) + (X' \cdot Y \cdot Z') \\ &= X \cdot Z + Y' \cdot Z + X' \cdot Y \cdot Z' \end{aligned}$$


 


Figure 4-12

Two-level AND-OR circuit.

Another equivalent

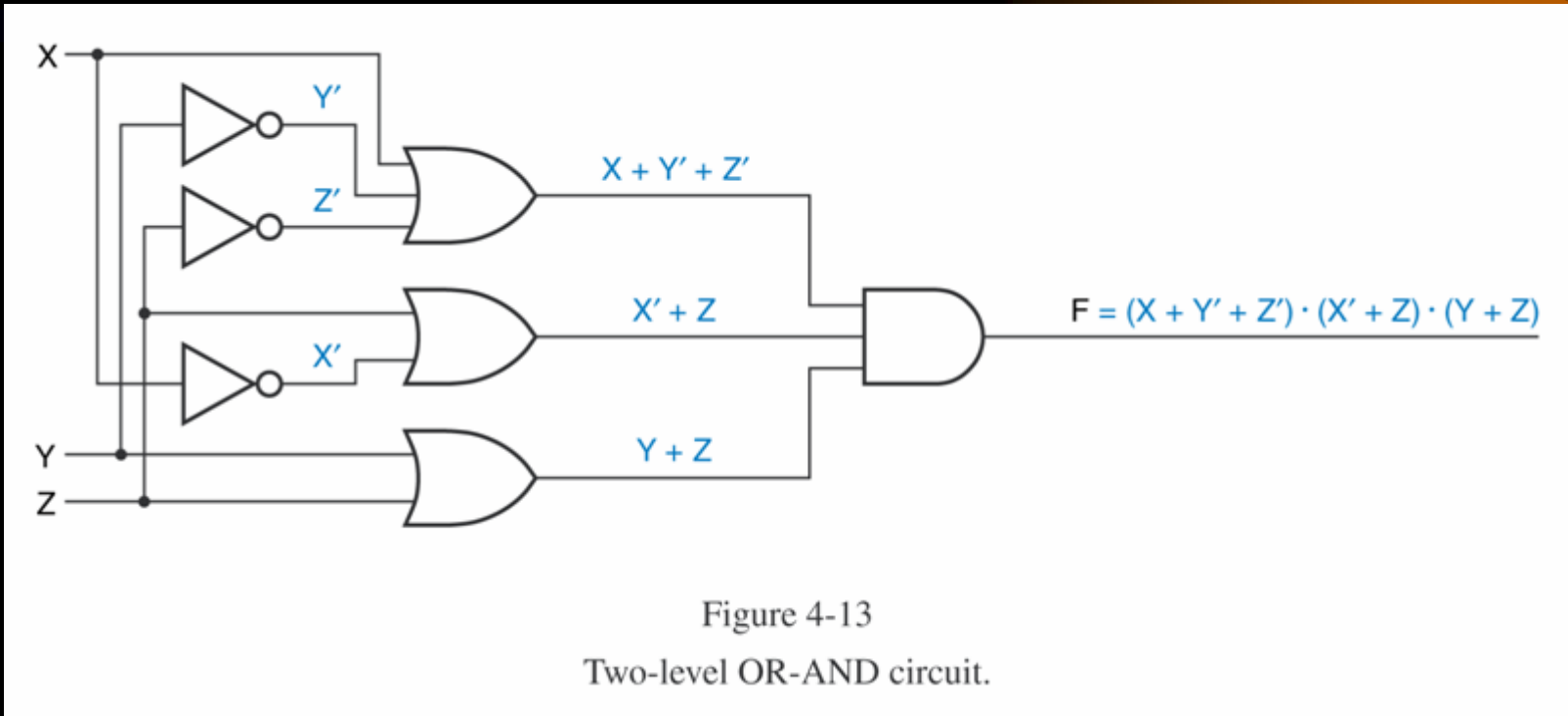

Circuit synthesis from “verbal” description

The ALARM output is 1 if the PANIC input is 1, or if the ENABLE input is 1, the EXITING input is 0, and the house is not secure; the house is secure if the WINDOW, DOOR, and GARAGE inputs are all 1.

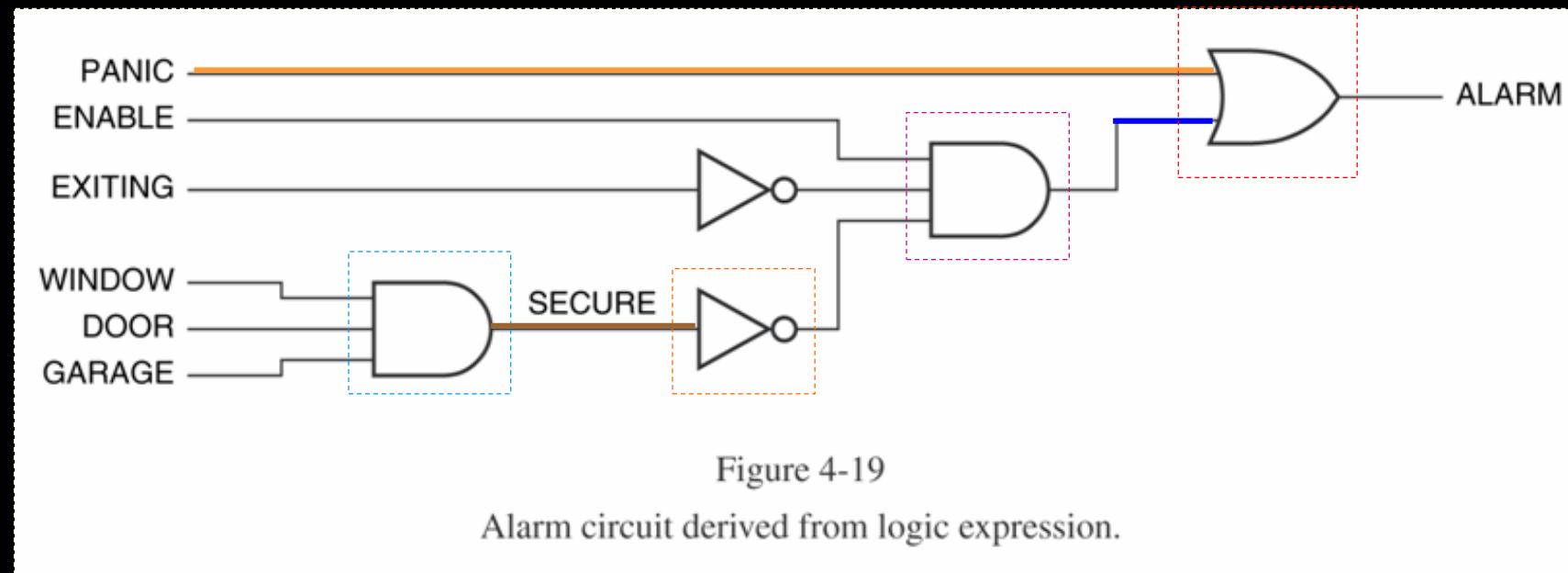


Figure 4-19

Alarm circuit derived from logic expression.

Sum-of-products equivalent

 


Figure 4-20

Sum-of-products version of alarm circuit.

Need for minimization



- ◆ A logic expression can be synthesized into a circuit in many different forms.
- ◆ Some of these forms are “better” than others
 - ✳ Fewer gates
 - ✳ Smaller gates (fewer inputs)
- ◆ Canonical SOP and POS realizations blow up quickly. Too many gates!
- ◆ We need to “minimize” our combinational circuits.

Typical minimization technique

◆ Generalization of the combining theorems, T10 and T10'

★ given product term $\cdot Y$ + given product term $\cdot Y' =$
given product term

★ (given sum term + Y) \cdot (given sum term + Y') =
given sum term

★ Each expression has been converted to a single term with one less variable.

● One gate has been eliminated, one fewer input



Prime number detector

- ◆ Given a 4-bit input combination

$N = N_3N_2N_1N_0$, produce a 1 output for
 $N=1, 2, 3, 5, 7, 11, 13$, and 0 otherwise.

- ◆ $F = \sum_{N_3, N_2, N_1, N_0} (1, 3, 5, 7, 11, 13)$
 $= N_3' \cdot N_2' \cdot N_1' \cdot N_0 + N_3' \cdot N_2' \cdot N_1 \cdot N_0$
 $+ N_3 \cdot N_2' \cdot N_1 \cdot N_0' + \dots$



Minimization

$$\begin{aligned} \blacklozenge F &= \sum_{N_3, N_2, N_1, N_0} (1, 3, 5, 7, 11, 13) \\ &= (N_3' \cdot N_2' \cdot N_1' \cdot N_0 + N_3' \cdot N_2' \cdot N_1 \cdot \\ &N_0) \\ &\quad + (N_3' \cdot N_2 \cdot N_1' \cdot N_0 + N_3' \cdot N_2 \cdot N_1 \cdot \\ &N_0) + \dots \\ &= N_3' \cdot N_2' \cdot N_0 + N_3' \cdot N_2 \cdot N_0 + \dots \\ &= N_3' \cdot N_0 + \dots \end{aligned}$$



Canonical sum design

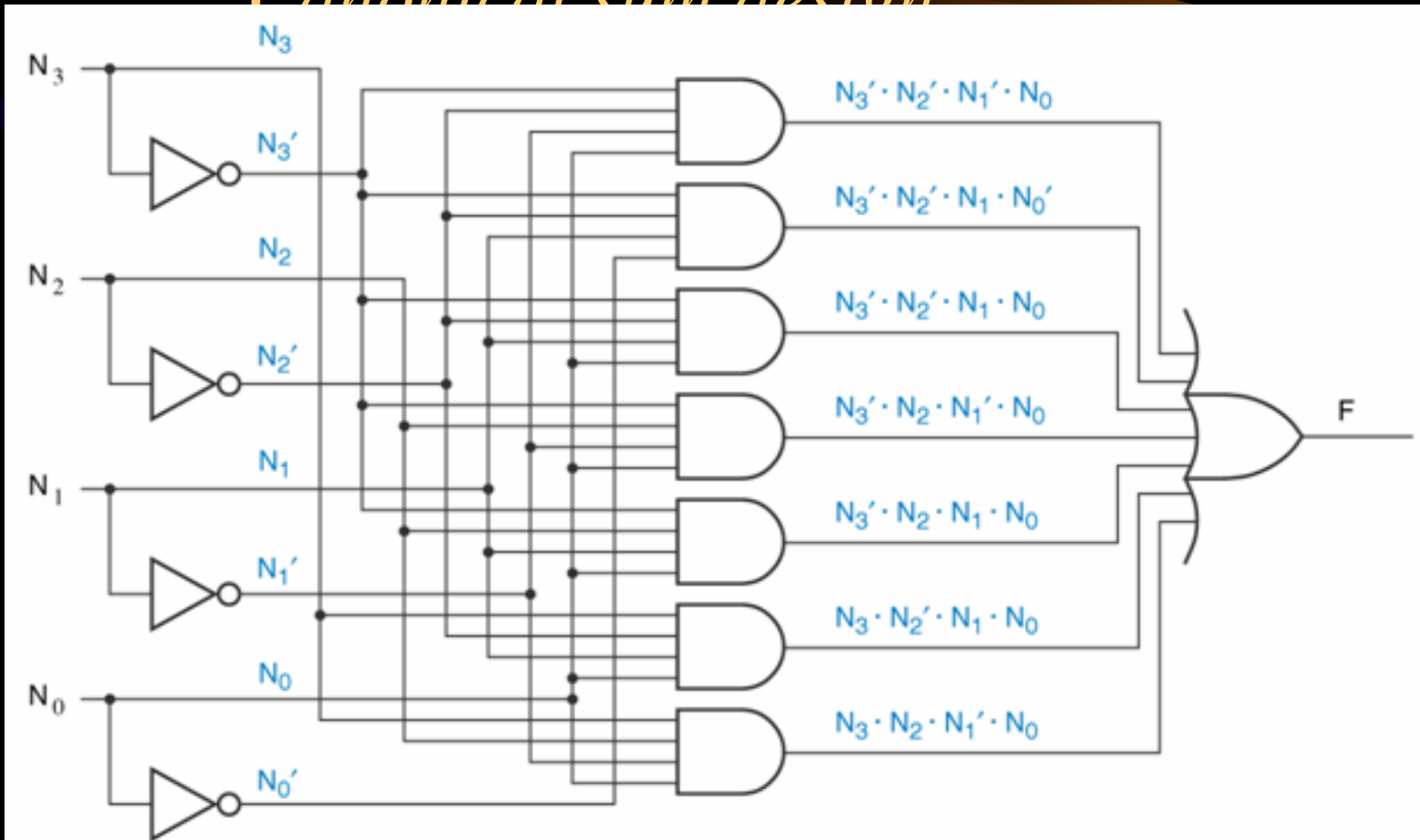


Figure 4-18

Canonical-sum design for 4-bit prime-number detector.



Minimized circuit

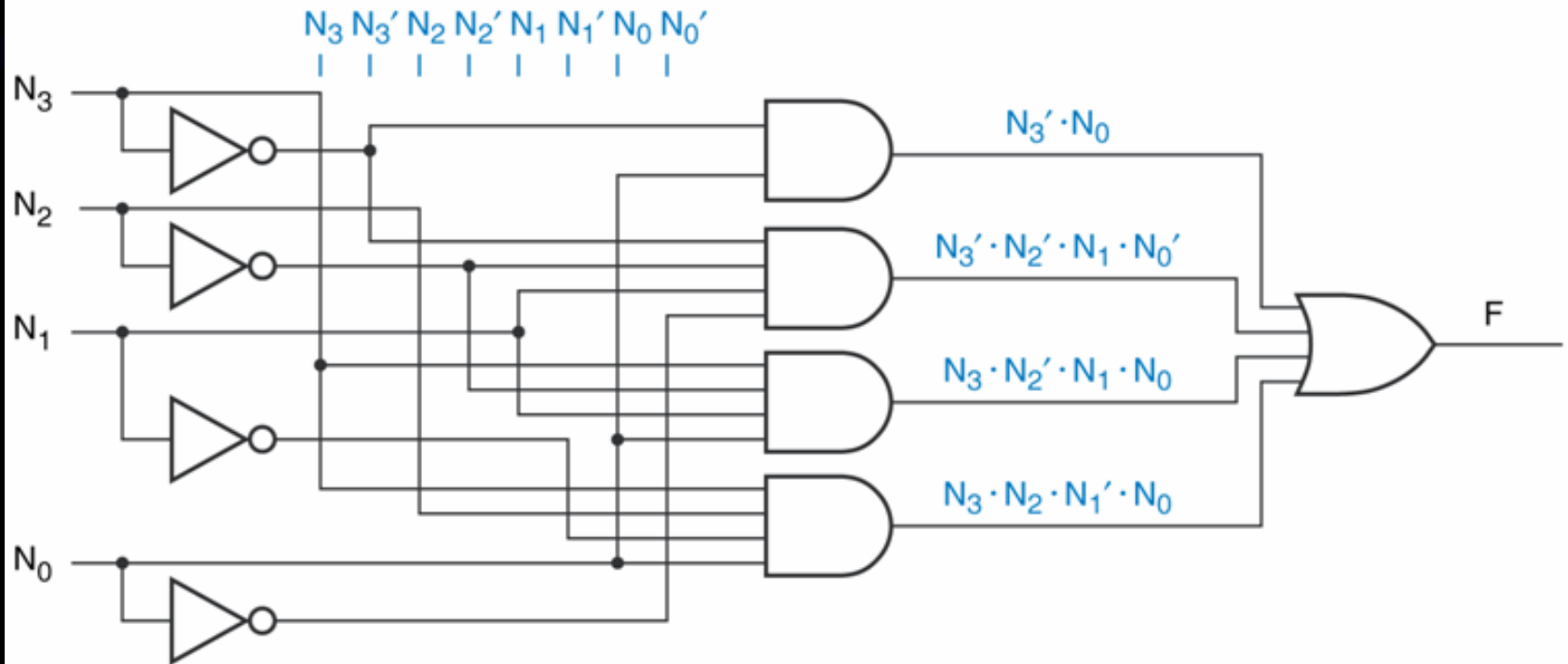


Figure 4-25

Simplified sum-of-products realization for 4-bit prime-number detector.



Karnaugh maps

 


Figure 4-26

Karnaugh maps: (a) 2-variable; (b) 3-variable; (c) 4-variable.



Examples

 


Figure 4-27

Karnaugh map for logic functions: (a) $F = \Sigma_{X,Y}(3)$;

(b) $F = \Sigma_{X,Y,Z}(0,3,4,6,7)$; (c) $F = \Sigma_{W,X,Y,Z}(1,2,3,5,7,11,13)$.



Minimization

 


Figure 4-28

$F = \Sigma_{X,Y,Z}(1,2,5,7)$: (a) truth table; (b) Karnaugh map; (c) combining adjacent 1-cells.

For cells 5 and 7:

$$F = \dots + X \cdot Y' \cdot Z + X \cdot Y \cdot Z$$

$$= \dots + X \cdot Z$$



Logic expression from K-map

- ◆ Mark rectangular sets of 2^i (wraparound allowed) 1 cells
- ◆ Literals of corresponding product terms can be determined directly from the map:
 - ★ If variable is 0 in every cell of marked area, then the variable is **complemented** in the product term
 - ★ If variable is 1 in every cell of marked area, then the variable is **uncomplemented** in the product term
 - ★ If variable is 0 in some cells of marked area and 1 in others, it does not appear in the product term
 - ★ A sum-of-products expression for a function must contain product terms (marked sets of 1-cells) that cover all of the 1's and none of the 0's on the map.



Product-of-sums expression

- ◆ By duality, carry out the same process for the K-map, this time grouping the 0's instead of the 1's.
- ◆ Each 0 on the map corresponds to a maxterm in the canonical product of the logic function.
- ◆ Entire process can be repeated.

