

CS 5803

*Introduction to High Performance Computer  
Architecture: Arithmetic Logic Unit*

A.R. Hurson

323 CS Building,

Missouri S&T

hurson@mst.edu

# *Introduction to High Performance Computer Architecture*



## ◆ Outline

- \* Motivation
- \* Design of a simple ALU
- \* How to design an ALU
- \* Fast ALU design
  - Fast Adder
  - Fast Multiplier
  - Fast Divider

## *Introduction to High Performance Computer Architecture*

Note, this unit will be covered in almost three weeks. In case you finish it earlier, then you have the following options:

- 1) Take the early test and start CS5803.module4
- 2) Study the supplement module  
(supplement CS5803.module3)
- 3) Act as a helper to help other students in studying CS5803.module3

Note, options 2 and 3 have extra credits as noted in course outline.

Enforcement of background

Glossary of prerequisite topics

Familiar with the topics?   
 No → Review Module   
 CS5803.module3.background

Yes

Take Test

Pass?   
 No → Remedial action

Yes

Glossary of topics

Familiar with the topics?   
 No → Take the Module

Yes

Take Test

Pass?   
 No → Take the Module

Yes

Options

Study next module?

Lead a group of students in this module (extra credits)?

Study more advanced related topics (extra credits)?

At the end: take exam, record the score, and impose remedial action if not successful

Extra Curricular activities

# *Introduction to High Performance Computer Architecture*

- ◆ You are expected to be familiar with:
  - ★ Representation of numbers,
  - ★ Basic arithmetic operations in digital systems, including: addition, multiplication, and division,
  - ★ Concept of serial, parallel, and modular ALU
- ◆ If not then you need to study `CS5803.module3.background`

## ◆ Arithmetic and Logic Unit (ALU)

- ★ In an attempt to improve the performance, this section will talk about the **Arithmetic Logic Unit**.
- ★ In regard to our earlier *CPU time*, we are looking at techniques to reduce  $p$ .

$$T = I_c * CPI * \tau = I_c * (p + m * k) * \tau$$

## ◆ Arithmetic and Logic Unit (ALU)

- ★ It is a functional box designed to perform **basic arithmetic, logic, and shift operations** on the data.
- ★ Implementation of the basic operations such as logic, program control, and data transfer operations are easier than arithmetic and I/O operations. Therefore, in this section we concentrate on arithmetic operations.



◆ Arithmetic and Logic Unit (ALU)

★ An ALU can be of three types:

- Serial
- Parallel (see `module3.background` for definitions and more discussion about serial and parallel ALU)
- Functional (Modular)





◆ Arithmetic and Logic Unit (ALU)

- ★ As discussed before a parallel ALU offers a higher speed relative to a serial ALU.
- ★ How can one improve the performance (speed) of ALU further?
- ★ Is it possible to build (design) an ALU faster than a parallel ALU?


## ◆ Arithmetic and Logic Unit (ALU)

### ★ Functional (modular) ALU

- ALU is a collection of **independent units** each tailored for a specific operation. As a result, **independent operations** can be overlapped.
- This approach allows an additional degree of concurrency relative to a parallel ALU, since it allows several operations to be performed on data simultaneously.
- This speed improvement comes at the expense of extra overhead needed to **detect data independent operations**.

◆ Arithmetic and Logic Unit (ALU)

★ Functional (modular) ALU

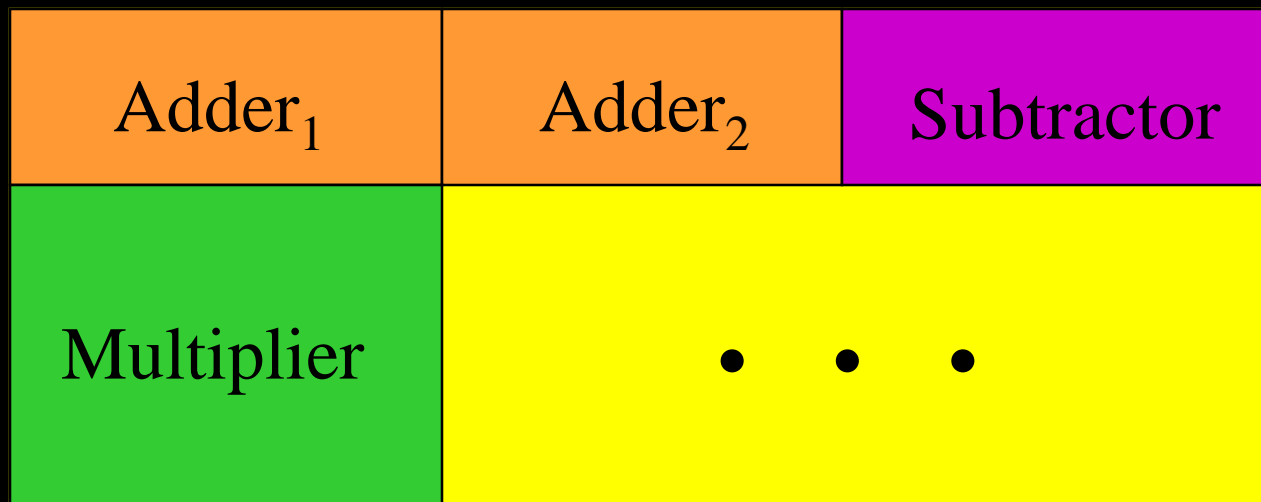

◆ Arithmetic and Logic Unit (ALU)

- ★ Is it possible to improve the performance of an ALU further?
- ★ Naturally, we can improve the performance (physical speed) by taking advantage of the advances in technology.
- ★ How can we improve the logical speed of the ALU further?

◆ Arithmetic and Logic Unit (ALU)

- ★ In a functional ALU, is it possible to devise algorithms which allow one to improve the performance of the basic operations?
- ★ If this is a valid direction, then the question of how to design a fast ALU will change to “how to design a fast adder, a fast multiplier, ...?”



◆ Question

- ★ As a computer architect, how do you design an ALU? In another words, in an attempt to design an ALU, what issues do you need to take into consideration?

## ◆ Fast Adder

- ★ How to design an adder faster than a parallel adder?
- ★ What is the major bottle-neck in a parallel adder?
- ★ Is the **carry generation** and **propagation** the major bottleneck?
- ★ Is it possible to **eliminate**, **moderate**, or **reduce** the delay of carry generation and propagation?



◆ Arithmetic and Logic Unit (ALU)

★ Carry Lookahead

● Scheme 1

● Scheme 2

★ Carry Select

★ Carry Lookahead plus Carry Select




◆ Fast Adder

- ★ Carry Lookahead — Generate and propagate carries ahead of time, relative to a parallel adder.

◆ Fast Adder

★ Basic Building Block — A 4-Bit Adder

 

◆ Fast Adder

★ Basic Building Block — A 4-Bit Adder (Timing)

$$F_1 = 4\Delta t \quad C_2 = 4\Delta t$$

$$F_2 = 6\Delta t \quad C_3 = 6\Delta t$$

$$F_3 = 8\Delta t \quad C_4 = 8\Delta t$$

$$F_4 = 10\Delta t \quad C_5 = 10\Delta t$$

◆ Fast Adder

★ Carry Lookahead (Scheme 1)

$$C_{i+1} = A_i B_i + (A_i \oplus B_i) C_i = A_i B_i + (A_i + B_i) C_i$$

Carry Generate term ( $G_i$ )

Carry Propagate Term ( $P_i$ )

◆ Fast Adder

★ Carry Lookahead (Scheme 1)

- In a 4-bit full adder

$$C_1 = 0$$

$$C_2 = g_1 + P_1 C_1$$

$$C_3 = g_2 + P_2 C_2 = g_2 + P_2 g_1 + P_2 P_1 C_1$$



$$C_4 = g_3 + P_3 C_3 = g_3 + P_3 g_2 + P_3 P_2 g_1 + P_3 P_2 P_1 C_1$$

$$C_5 = \dots$$

# Introduction to High Performance Computer Architecture

## ◆ Fast Adder — Carry Lookahead (Scheme 1)

### ★ Extended 4-Bit Full Adder

  

◆ Fast Adder — Carry Lookahead (Scheme 1)

★ Extended 4-Bit Full Adder — Timing



$$d \cong 2\Delta t$$

$p^s$  and  $g^s$  are generated in  $d$

$C^s$  are generated after another  $d$

$F^s$  are generated after another  $d$

 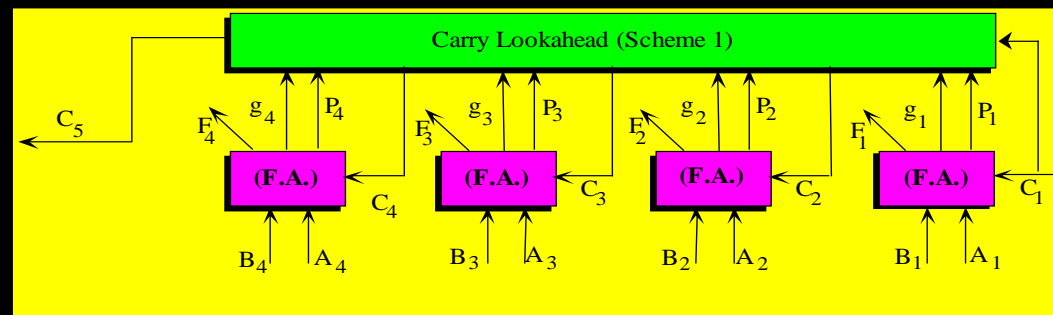
## ◆ Fast Adder — Carry Lookahead (Scheme 1)





# Introduction to High Performance Computer Architecture

 
## ◆ Fast Adder — Carry Lookahead (Scheme 2)



Timing

$$CLA = 5\Delta t$$

 Cascades of CLAs overlap  $1\Delta t$  operation





## ◆ Fast Adder

### ★ Carry Select

- Carry-in to a 4-bit full adder is either 0 or 1.
- Duplicate each stage - e.g., 4-bit full adder.
- Initiate each unit in a stage with carry-in of 0 and 1.
- Use a multiplexer to select the correct answer.

# Introduction to High Performance Computer Architecture

## ◆ Fast Adder — Carry Select

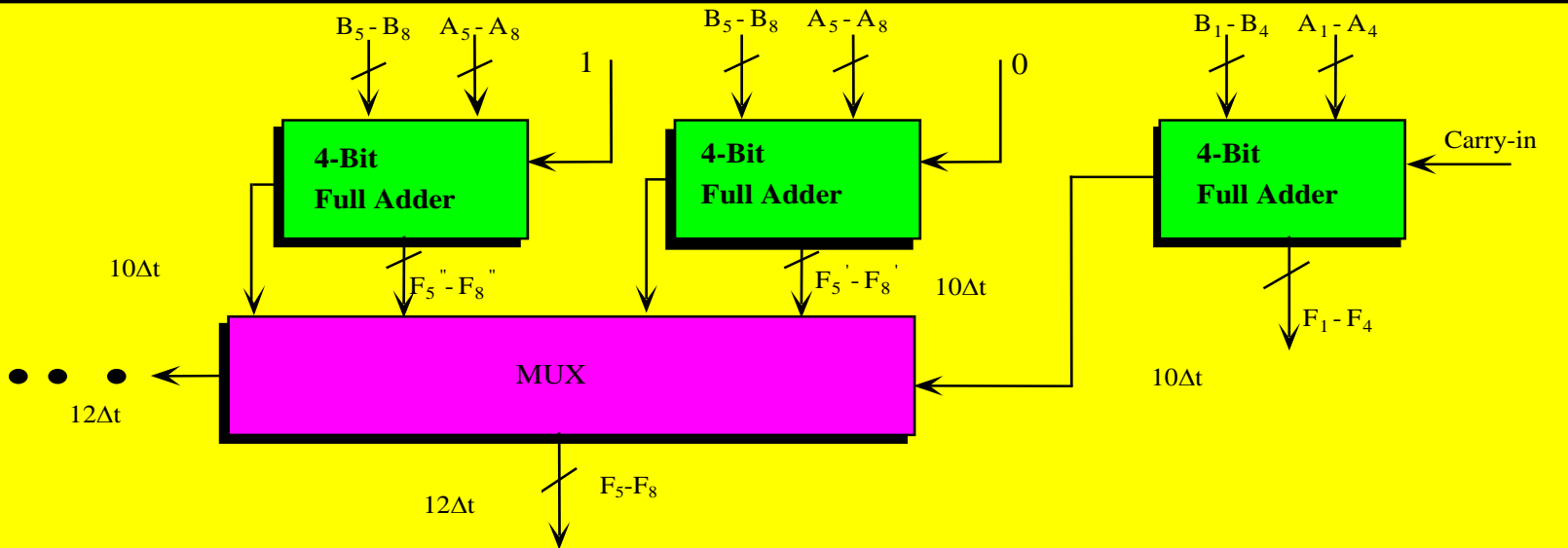 

## ◆ Questions

- ★ Calculate the execution time of a 16-bit adder using carry lookahead scheme 1.
- ★ Formulate the execution time of an  $n$ -bit adder using carry lookahead scheme 1 ( $n$  is a multiple of 4).
- ★ Calculate the execution time of a 16-bit adder using carry lookahead Scheme 2.
- ★ Formulate the execution time of an  $n$ -bit adder using carry lookahead scheme 2 ( $n$  is a multiple of 4).

## ◆ Questions


- ★ Calculate the execution time of a 16-bit adder using carry select scheme.
- ★ Formulate the execution time of an  $n$ -bit adder using carry select scheme.
- ★ Is it possible to combine carry lookahead and carry select concepts to design a faster adder?

## ◆ Multiplication

- ★ Multiplication can be performed as a sequence of repeated additions.
- ★  $A * B$  is interpreted as add  $A$ ,  $B$  times. However, such a scheme is very inefficient with a time complexity of  $O(m)$  where  $m$  is the magnitude of  $B$ .
- ★ A better approach to multiplication, **add-and-shift**, produces a time complexity of  $O(n)$  where  $n$  is the length of the  $B$ .

◆ **Add-and-shift** — hardware configuration

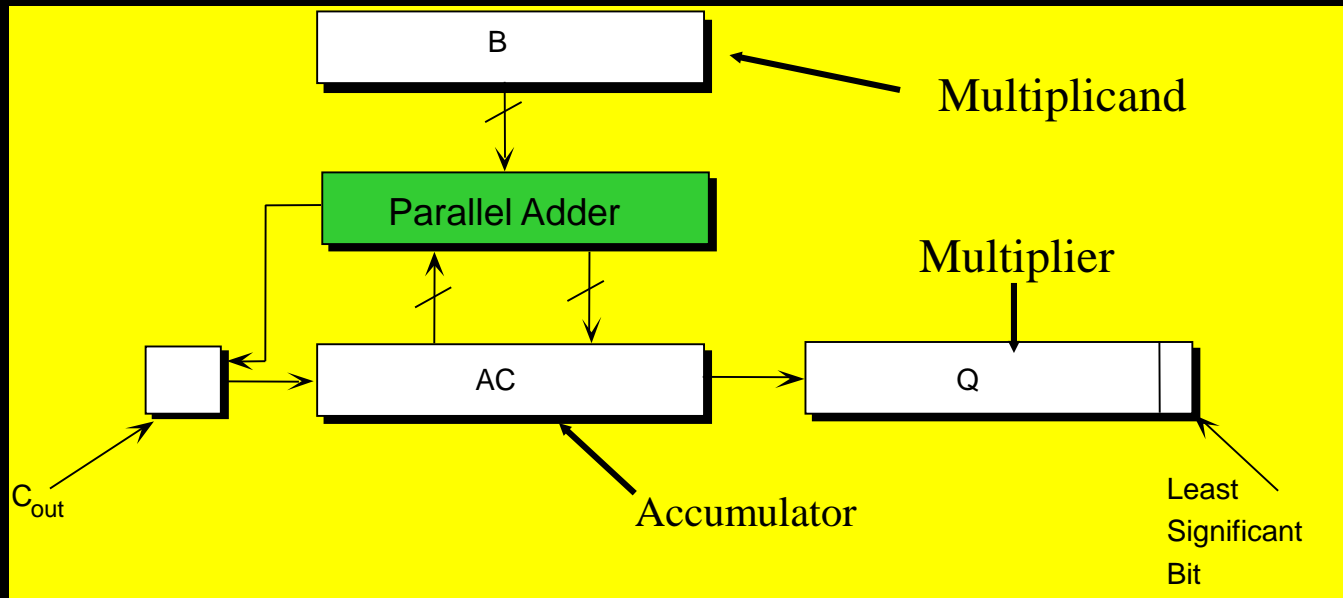- ★ Multiplier and multiplicand are two  $n$ -bit unsigned numbers,
- ★ Result is a  $2n$ -bit number stored in an accumulator and multiplier registers.



## ◆ Add-and-shift — Algorithm

- ★ In each iteration the least-significant bit of multiplier is checked;
  - if one, then multiplicand is added to the accumulator and the contents of accumulator and multiplier is shifted right one position.
  - if zero, just shift accumulator and multiplier to the right.
  - See module3.background for additional discussion about Add-and-shift algorithm.



## ◆ Multiplication — Booth's Algorithm

- ★ Booth's algorithm is an extension to the **add-and-shift** approach.
- ★ In each iteration two bits of multiplier are being investigated and proper action(s) will be taken according to the following coding table:

00	no action	shift right once
01	add multiplicand	shift right once
10	sub multiplicand	shift right once
11	no action	shift right once

See module3.background for more discussion about Booth's algorithm.

◆ Multiplication — Modified Booth's Algorithm

★ Check 3 bits of multiplier at a time and take proper steps as follows:

000	no action	shift right twice
001	add multiplicand	shift right twice
010	add multiplicand	shift right twice
011	add 2*multiplicand	shift right twice
100	sub 2*multiplicand	shift right twice
101	sub multiplicand	shift right twice
110	sub multiplicand	shift right twice
111	no action	shift right twice

## ◆ Multiplication — Booth's Algorithm

- ★ Any version of Booth's algorithm allows a sequence of consecutive 1<sup>s</sup> to be bypassed.
- ★ Modified Booth's Algorithm is faster than Booth's Algorithm.
- ★ Booth's Algorithm can be further extended by looking at 4 bits, (5 bits, ...) at a time and taking proper actions according to the proper encoding table.

## ◆ Multiplication — Modified Booth's Algorithm

001011 * 011001	Extension	
000000 0110010	←	
001011		010 ⇒ add B, shift twice
001011 0110010		
000010 1101100		100 ⇒ sub 2B, shift twice
101010		
101100 1101100		
111011 0011011		011 ⇒ add 2B, shift twice
010110		
010001 0011011		
000100 010011 0		
Answer ↗		

## ◆ Summary

- ★ How to design an ALU?

- ★ Fast adder

  - Carry Lookahead

  - Carry Select

- ★ Multiplication

  - Add-and-shift

  - Booth's algorithm and its extension

## ◆ Multiplication

★ The **add-and-shift** algorithm can be used to multiply numbers (say  $A$  and  $B$ ) in  $2^s$  complement, if the result is adjusted properly. Three cases can be recognized.

- Case 1: **A positive; B negative**
- Case 2: **A negative; B positive**
- Case 3: **A negative; B negative**

◆ Multiplication — Case 1: A positive B negative

★ Proof

$$A * \tilde{B} = A * (2^n - B) = 2^n A - A * B$$

$$A * B = 2^n A - A * \tilde{B}$$

$$2^{2n} - A * B = 2^{2n} - 2^n A + A * \tilde{B}$$

$$\tilde{A}\tilde{B} = 2^n(2^n - A) + A * \tilde{B} = 2^n \tilde{A} + A * \tilde{B}$$

Multiply A and B using **add-and-shift** algorithm and adjust the result by  $2^n \cdot \tilde{A}$



◆ Questions

- ★ Justify case 2 and case 3.
- ★ Is it possible to use the same technique for 1<sup>s</sup> complement numbers?



◆ Multiplication — Example

★ Perform  $00101 * 11010$  using add-and-shift algorithm, numbers are in  $2^s$  complement format:

# Introduction to High Performance Computer Architecture

E	AC	A	
0	00000	11010	$A_n = 0$ , shift right EACA
0	00000	01101	$A_n = 1$ , add B
	00101		
<hr/>			
0	00101	01101	Shift right EACA
0	00010	10110	$A_n = 0$ , shift right EACA
0	00001	01011	$A_n = 1$ , add B
	00101		
<hr/>			
0	00110	01011	Shift right EACA
0	00011	00101	$A_n = 1$ , add B
	00101		
<hr/>			
0	01000	00101	Shift right EACA
0	00100	00010	Adjust the result
	11011		
<hr/>			
	11111	00010	← Answer


## ◆ Fast Multiplication

### ★ Reduction of Summands

- Generate **matrix of summands** (partial products).
- Go over several **reduction stages** using 2-2 and 3-2 adders.
- In final stage (2 rows) use a **fast adder** to generate the result.



# Introduction to High Performance Computer Architecture
 
## ◆ Fast Multiplication — Reduction of Summands



# Introduction to High Performance Computer Architecture
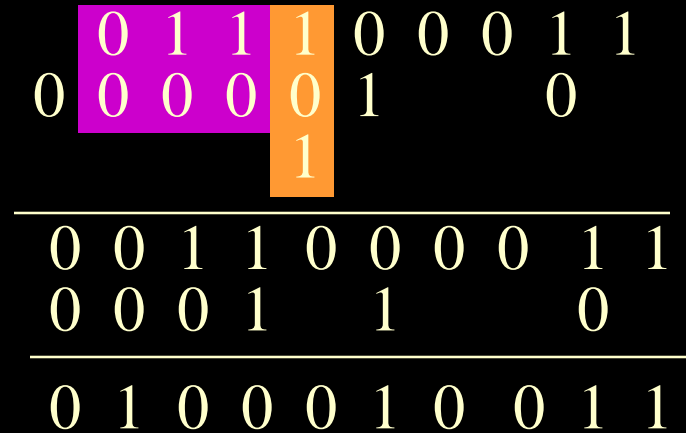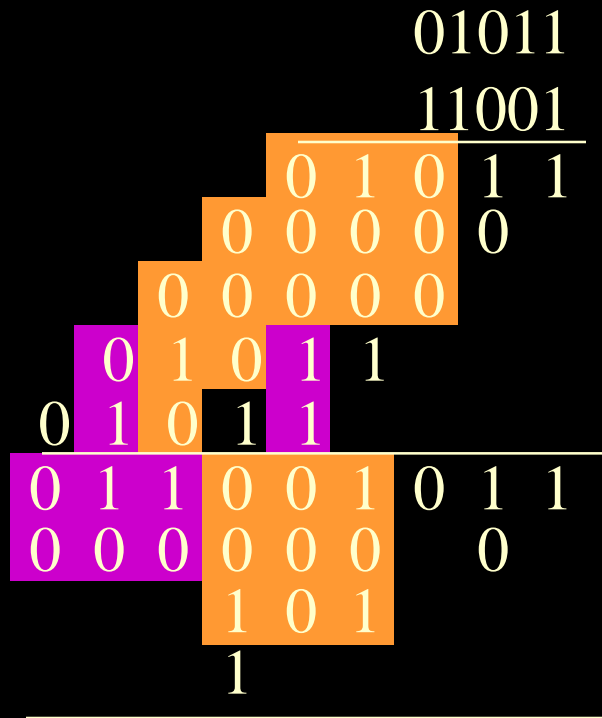
## ◆ Fast Multiplication — Reduction of Summands





◆ Summary

★ Multiplication

- Add-and-shift
- Booth's algorithm and its extension

★ Reduction of Summands

## ◆ Fast Multiplication — Reduction of Summands

- ★ It is suitable for unsigned numbers.
- ★ Number of reduction stages depends on the length of the multiplier.
- ★ Execution time:

$$T_{RS} = \Delta t + m * (4 \Delta t) + P$$

Time to generate matrix of summands      No. of reduction stages      Execution time of the fast adder

## ◆ Fast Multiplication

### ★ Iterative Method

- Multiplication of 2  $n$ -bit numbers can be converted into **four multiplications** of  $n/2$ -bit numbers and **two additions**.
- This scheme can be **iteratively** applied to all multiplication terms




◆ Fast Multiplication — Iterative Method

$$X = 2^{n/2} a + b, Y = 2^{n/2} c + d$$

$$X * Y = (2^{n/2} a + b) * (2^{n/2} c + d) = 2^n (ac) + 2^{n/2} (ad + bc) + bd$$

◆ Fast Multiplication — Iterative Method

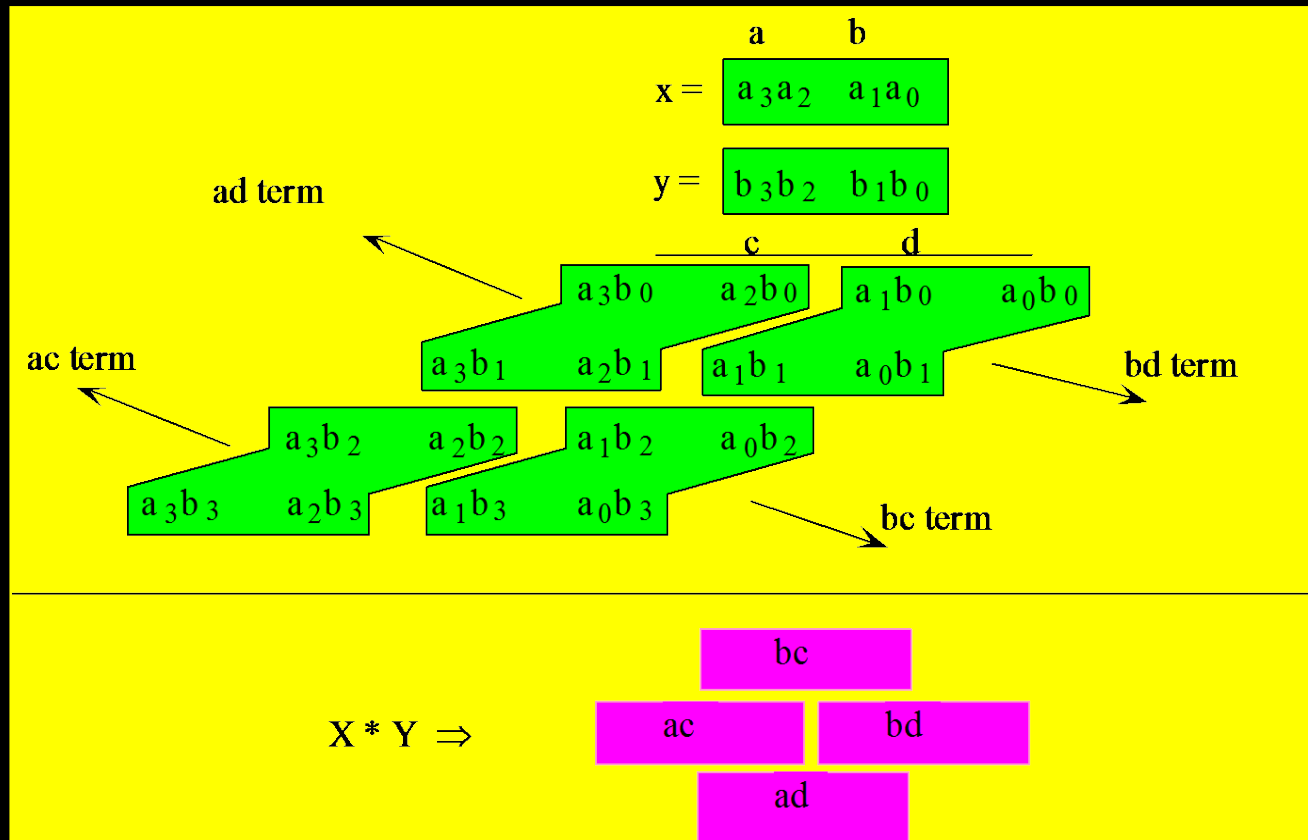

## ◆ Fast Multiplication

### ★ Iterative Method — An Example

$$x = a_3a_2a_1a_0$$

$$y = b_3b_2b_1b_0$$


$$x * y = 2^4(a_3a_2)(b_3b_2) + 2^2[(a_3a_2)(b_1b_0) + (a_1a_0)(b_3b_2)] + (a_1a_0)(b_1b_0)$$

## ◆ Fast Multiplication


### ★ Iterative Method — An Example

$$x = 1010$$

$$y = 1100$$

 
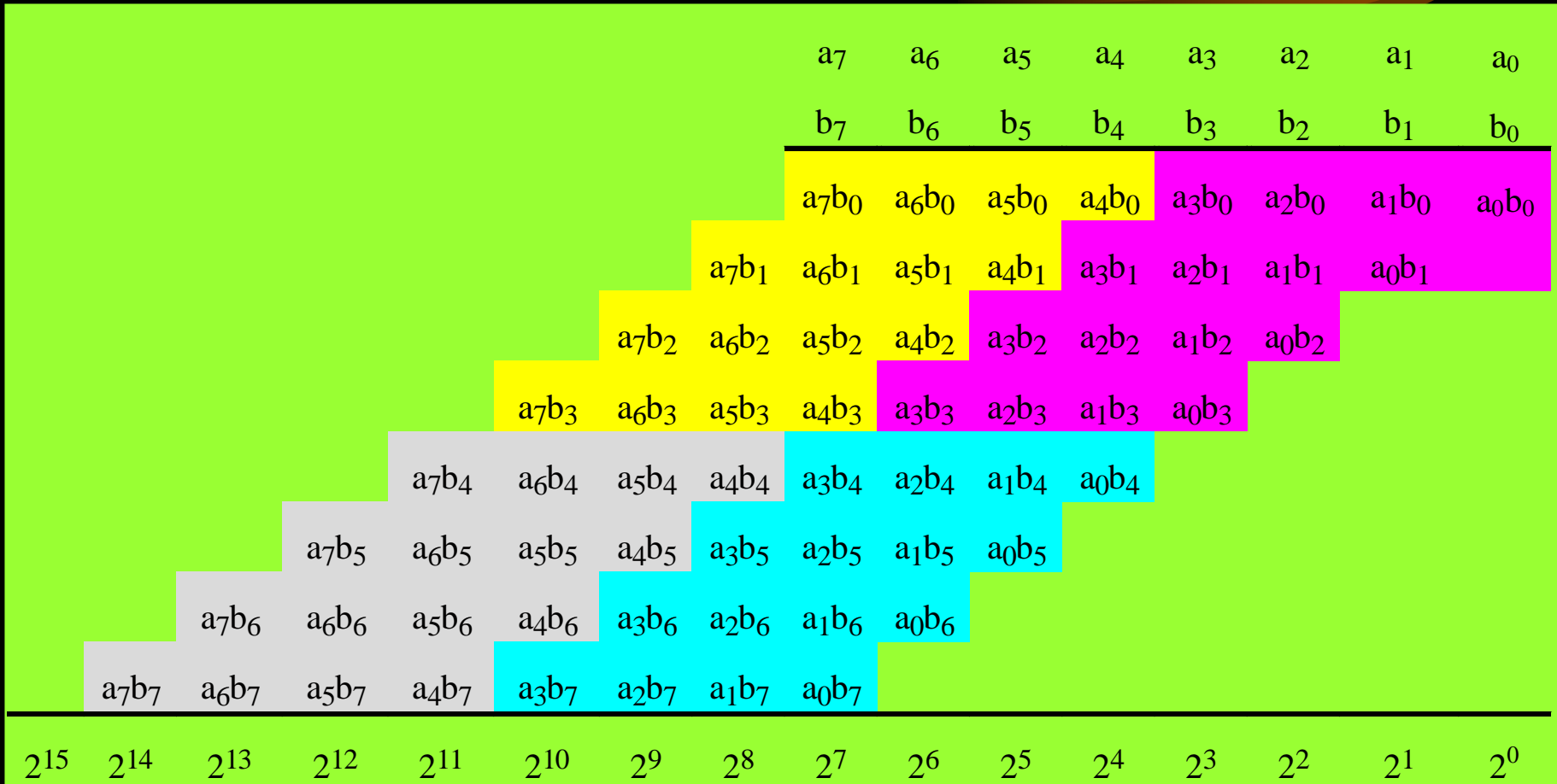
# Introduction to High Performance Computer Architecture



## ◆ Fast Multiplication

### ★ Hurson's Scheme — Observations

- In a parallel multiplier unit first an  $n \times n$  matrix of partial products ( $M$ ) is generated and then elements in each column are added.

$$m_{ij} \in M \begin{cases} 1 & \text{if } B_i = Q_j = 1 \quad 1 \leq i, j \leq n \\ 0 & \text{otherwise} \end{cases}$$

## ◆ Fast Multiplication

### ★ Hurson's Scheme — Observations

- An element  $m_{ij}$  in  $M$  is the result of an AND operation between the  $i^{\text{th}}$  bit of multiplicand and  $j^{\text{th}}$  bit of multiplier.
- In each column, zero elements do not affect the summation in that column and carry to the next column.
- Each pair of  $1^{\text{s}}$  in a column contributes a carry to the next column.
- The result of summation for each column is either zero (even number of  $1^{\text{s}}$ ) or one (odd number of  $1^{\text{s}}$ ).

◆ Fast Multiplication — Hurson's Scheme

- ★ Generate only non-zero elements in each column.
- ★ For each pair of 1<sup>s</sup> in a column generate a carry to the next column.
- ★ Count the number of 1<sup>s</sup> in each column.



## ◆ Fast Multiplication

### ★ Hurson's Scheme — Example

B = 11010	
*Q = 11011	
<hr/>	
111111110	← Matrix of partial products without zero elements
1  11	
1	
<hr/>	
1 111111110	← Generate carries
11111	
1  11	
<hr/>	
1 01011 1110	← Count the number of 1s in each column




◆ Fast Multiplication

★ Full Adder Tree

- Generate matrix of summands.
- Use a binary tree of full-adders to calculate the result in a pipeline fashion

◆ Fast Multiplication — Full Adder Tree

 

## ◆ Questions

- ★ For an  $n * n$  multiplication, calculate the execution time of the operation using **full adder tree** scheme.
- ★ Show the "snap shots" of the events to perform:  
 $1101 * 1011$  using **full adder tree** scheme.


◆ Fast Multiplication — Column Compression

- ★ Assume that a population counter is available that can count the number of 1<sup>s</sup> in an n-bit word, producing a  $1 + \lfloor \log_2 n \rfloor$  bit result.
- ★ Similar to the reduction of summands technique one can go through several reduction stages to compress the number of bits in each column.


◆ Fast Multiplication — Column Compression

- ★ Generate matrix of summands.
- ★ Go over several stages using population counters.
- ★ In final stage (2 elements in each column) use a fast adder to generate the result.

 ◆ Fast Multiplication — Column Compression



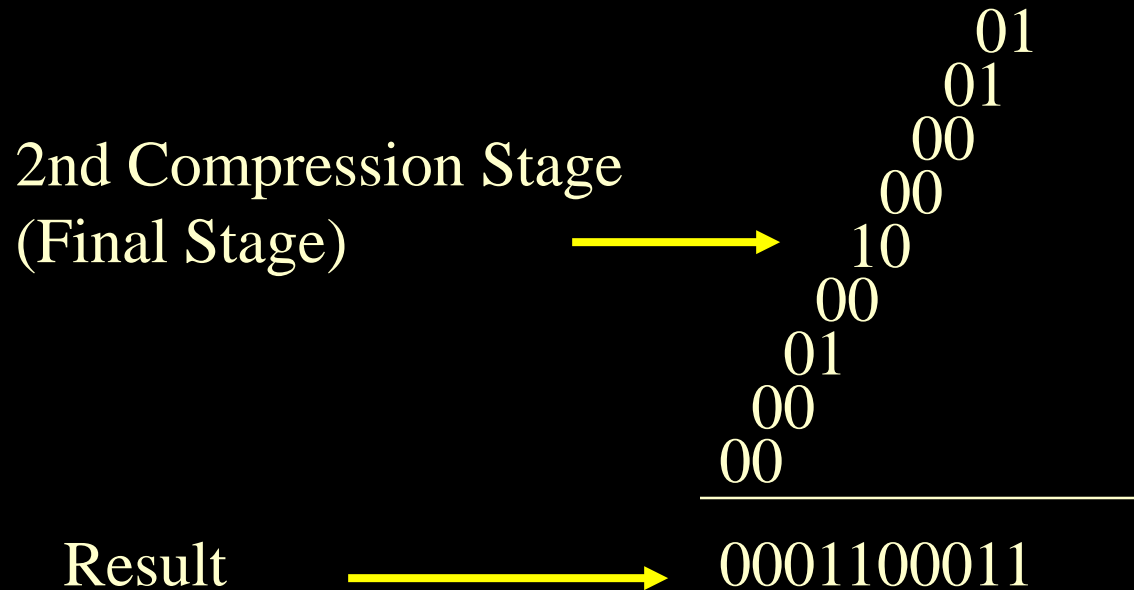◆ Fast Multiplication — Column Compression







◆ Question

- ★ Formulate the execution time of an  $n * n$  multiplier unit using column compression scheme.

## ◆ Division

- ★ Similar to multiplication, one can develop a routine to perform division as a **sequence of subtractions**.
- ★ However, such an algorithm is very inefficient and slow.
- ★ Instead one can develop an algorithm which performs division as a sequence of Compare, **Shift** and **Subtract** operations.

## ◆ Division

- ★ One should note that division in a binary system is much simpler than the division in decimal system, since the quotient digits are either 0 or 1.
- ★ To **minimize the hardware requirements**, we should remember that:
  - Comparison can be performed via arithmetic operation (s).
  - Subtraction can be performed via complement-addition.
- ★ In other words; division requires almost the same hardware modules as multiplication does.

## ◆ Division

- ★ Division can be carried out as a sequence of  $n$  iterations.
- ★ Dividend is a double register.
- ★ One bit of the quotient is generated in each iteration.
- ★ At the end of the operation, the quotient is in the 1st half part of the double register (low-order part), and remainder is in the 2nd half part.
- ★ Sign of the quotient is the X-OR of the signs of dividend and divisor.
- ★ Sign of the remainder is the same as the sign of the dividend.



## ◆ Division

### ★ Methods of Division

- There are several different algorithms for division:
  - Restoring Method
  - Non-Restoring Method
  - Direct Comparison

◆ Fast Division — SRT Method

- ★ Faster direct division can be developed on **normalized numbers** by observing sequences of more than one bit of the dividend or partial remainder - i.e., **sequences of 0<sup>s</sup> and 1<sup>s</sup> can be skipped.**
- ★ This method was proposed to improve binary floating-point arithmetic.

## ◆ Fast Division — SRT Method

### ★ Assumptions

- The dividend and divisor are **binary fractions**.
- The divisor (B) is an n-bit **normalized number** — i.e.,  $B = .1b_{n-2} \dots b_1b_0$ ,  $.5 \leq B < 1$ .
- The dividend-quotient (AQ) combination is a 2n-bit register - i.e.,

$$AQ = \underbrace{.00 \dots 0}_{k \text{ Zeros}} \quad 1 a_{n-(k+2)} \quad a_1 a_0 q_{n-1} \dots q_1 q_0$$



◆ Fast Division — SRT Method

★ Assumptions

- The dividend is normalized during the division operation.
- Divide overflow condition will be detected and steps are taken in order for it to be overcome.



◆ Fast Division — **SRT Method**

- ★ The divisor is normalized and the dividend-quotient combination is adjusted by shifting it left the same number of positions that the divisor was shifted during normalization.
- ★ This step allows that the relative magnitudes of divisor and dividend remain the same.

◆ Fast Division — **SRT Method**

- ★ AQ is normalized — i.e., for each shift left a 0 is inserted for  $q_0$  — Skipping over zeros.

$$\text{AQ} = .1 \ a_{n-2} \ \dots \ a_1 \ a_0 \ q_{n-1} \ \dots \ q_k \ \underbrace{00 \ \dots \ 0}_{\text{K Zeros}}$$

- ★ After this step, repeat the following sequence of steps:

◆ Fast Division — SRT Method

★ Subtract divisor from the dividend:

- If **positive result**, a 1 is inserted for  $q_0$  and left shift AQ register.

◆ Fast Division — SRT Method

- If negative result - i.e.,

$$AQ = 1.1 \dots a_1 a_0 q_{n-1} \dots \overbrace{00 \dots 0}^k$$

- Insert 0 for  $q_0$  and shift left AQ register
- Shift over  $1^s$ , and insert  $1^s$  until

$$AQ = 1.0 \dots a_1 a_0 q_{n-1} \dots \overbrace{0 \dots 0}^{k+1} \overbrace{111 \dots 1}^m$$

- Add B to A and shift AQ to left

◆ Fast Division — SRT Method

★ Perform the following operation

$$\begin{array}{r} \text{A} \quad \text{Q} \\ \text{AQ} = .00000 \ 10111 \quad (23 * 2^{-10}) \\ \text{B} = .00101 \quad (5 * 2^{-5}) \\ \text{Normalized B} = .10100 \\ \hline \text{Normalized B} = 1.01100 \end{array}$$

◆ Fast Division — SRT Method

	.00000	10111
Adjust AQ	.00010	111**
Shift over 0 <sup>s</sup>	.10111	**000
Subtract B	<u>1.01100</u>	
Positive Result:	0.00011	**000
Shift AQ left, q <sub>0</sub> ← 1	.0011*	*0001
Shift over 0 <sup>s</sup>	<u>.11**0</u>	<u>00100</u>

Remainder

Quotient

◆ Fast Division — SRT Method

$$\begin{array}{rcc} & A & Q \\ AQ = & .00001 & 10111 & (55 * 2^{-10}) \\ B = & .01010 & & (10 * 2^{-5}) \\ \text{Normalized B} = & .10100 & & \\ \hline \text{Normalized B} = & 1.01100 & & \end{array}$$

◆ Fast Division — SRT Method

	.00001	10111
Adjust AQ	.00011	0111*
Shift over 0 <sup>s</sup>	.11011	1*000
Subtract B	<u>1.01100</u>	
Positive Result:	0.00111	1*000
Shift AQ left, q <sub>0</sub> ← 1	.01111	*0001
Shift over 0 <sup>s</sup>	.1111*	00010
Subtract B	<u>1.01100</u>	
Positive Result:	0.0101*	00010
Shift AQ left, q <sub>0</sub> ← 1	.101* 0	00101



◆ Fast Division — **SRT Method**

$$\begin{array}{r} \text{A} \quad \text{Q} \\ \text{AQ} = .00101 \quad 00100 \\ \text{B} = .01111 \\ \text{Normalized B} = .11110 \\ \hline \text{Normalized B} = 1.00010 \end{array}$$

◆ Fast Division — SRT Method

	.00101	00100
Adjust AQ	.01010	0100*
Shift over 0 <sup>s</sup>	.10100	100*0
Subtract B	<u>1.00010</u>	
Negative Result:	1.10110	100*0
Shift AQ left, $q_0 \leftarrow 0$	1.01101	00*00
Add B	<u>.11110</u>	
Positive Result:	0.01011	00*00
Shift AQ left, $q_0 \leftarrow 1$	.10110	0*001
Subtract B	<u>1.00010</u>	
Negative Result:	1.11000	0*001

◆ Fast Division — SRT Method

Negative Result:	1.11000	0*001
Shift AQ left, $q_0 \leftarrow 0$	1.10000	*0010
Shift over 1 <sup>s</sup>	1.0000*	00101
Add B	<u>.11110</u>	
Negative Result:	1.1111*	00101
Shift AQ left, $q_0 \leftarrow 0$	1.111*0	01010
Correct remainder by shifting A and adding B	1.1111*	
	<u>.11110</u>	
	0.1110*	

quotient

Remainder

◆ Fast Division — Divisor Reciprocation

- ★ This method generates the reciprocal of the divisor using an iterative process, and then obtains the quotient by multiplying the dividend by the divisor reciprocal

$$A/B = A * (1/B)$$

◆ Fast Division — Divisor Reciprocation

- ★ The divisor ( $B$ ) is assumed to be a positive and normalized number,

$$1/2 \leq B < 1 \Rightarrow 1 < 1/B \leq 2$$

- ★ An initial value  $X_0 \approx 1/B$  is determined using a ROM table or a combinational logic circuit,

$$B = .1b_2b_3 \dots b_n \Rightarrow X_0 = 1.d_1d_2 \dots d_n$$

◆ Fast Division — Divisor Reciprocation

- ★ Then the following iterative cycles will be performed to determine the inverse value with reasonable accuracy

$$a_0 = B x_0 \quad \left\{ \begin{array}{l} x_1 = x_0 (2 - a_0) \\ a_1 = a_0 (2 - a_0) \end{array} \right. , \quad \left\{ \begin{array}{l} x_2 = x_1 (2 - a_1) \\ a_2 = a_1 (2 - a_1) \end{array} \right. , \quad \left\{ \begin{array}{l} x_n = x_{n-1} (2 - a_{n-1}) \\ a_n = a_{n-1} (2 - a_{n-1}) \end{array} \right.$$

- ★ The number of iterations (n) will be chosen to satisfy the following relation:

$$|1 - B x_n| \leq \epsilon$$

Relative error

◆ Fast Division — Divisor Reciprocation

★ Assume  $B = .75 \Rightarrow 1/B = 1.3333 \dots$

★ Take  $X_0 = 1$ , naturally  $X_0$  is not the exact inverse of  $B$  and the error is  $\delta = .333333\dots$

$$X_1 = X_0 (2 - BX_0) = 1 (2 - .75) = 1.25 \quad \delta = .08333\dots$$

$$X_2 = X_1 (2 - BX_1) = 1.25 (2 - .75 * 1.25) = 1.328125 \\ \delta = .005208333\dots$$

$$X_3 = X_2 (2 - BX_2) = 1.328125 (2 - .75 * 1.32815) \\ = 1.333313 \quad \delta = .000020333\dots$$

Newton's Method

◆ Fast Division — Multiplicative Division

★ The operation of division is replaced by that of finding a factor  $F$  such that:

$$B * F = 1 \text{ and } A * F = Q$$

★ An **iterative method** can be used to determine  $F$ .



◆ Fast Division — **Multiplicative Division**

- ★ In each iteration a constant factor (**multiplying factor**)  $F_i$  ( $1 \leq i \leq n$ ) is calculated to converge the denominator (Divisor) rapidly toward 1.

$$Q = \frac{A * F_0 * F_1 * \dots * F_n}{B * F_0 * F_1 * \dots * F_n}$$

◆ Fast Division — Multiplicative Division

- ★ The **numerator** (dividend) and the **denominator** (divisor) are both positive fractions.
- ★ The divisor is a normalized number and the dividend is shifted accordingly.

$$1/2 \leq B < 1, \quad B = 1 - \delta \quad \Rightarrow \quad 0 < \delta \leq 1/2$$

◆ Fast Division — **Multiplicative Division**

★  $F_i^s (0 \leq i \leq n)$  are chosen such that  $B_{i-1} < B_i$ ,

Where

$$\begin{aligned} B_0 &= B * F_0 \\ B_1 &= B * F_0 * F_1 \\ &\vdots \\ &\vdots \\ B_{i-1} &= B * F_0 * F_1 * \dots * F_{i-1} \\ B_i &= B * F_0 * F_1 * \dots * F_{i-1} * F_i \\ &\vdots \\ &\vdots \\ B_n &= B_{n-1} * F_n \end{aligned}$$

◆ Fast Division — Multiplicative Division

★  $B = 1 - \delta \Rightarrow F_0 = 1 + \delta$ , hence:

$$B_0 = (1 - \delta)(1 + \delta) = 1 - \delta^2 \Rightarrow B_0 \text{ is closer to } 1 \text{ than } B$$

★  $F_1 = 1 + \delta^2$  hence:

$$B_1 = B_0 * F_1 = (1 - \delta^2)(1 + \delta^2) = (1 - \delta^4)$$

⋮

$$F_i = 1 + \delta^{2^i}$$

◆ Fast Division — Multiplicative Division

★ Note: The initial multiplying factor ( $F_0$ ) can be obtained by a table look up.

★ Note: Since we are dealing with binary numbers

$$F_i = 1 + \delta^{2^i} = 2 - (1 - \delta^{2^i}) = 2 - \overline{B_{i-1}} = \overline{\overline{B_{i-1}}}$$

◆ Fast Division — Multiplicative Division

- ★ For each iteration two multiplications are required:
  - One to process the next denominator from which the next multiplying factor is obtained, and
  - One that produces the next numerator.

◆ Fast Division — Multiplicative Division

$F_0$  Obtain

$$F_1 = \tilde{B}_0$$

$$F_2 = \tilde{B}_1$$

$$B_0 = B * F_0$$

$$B_1 = B_0 * F_1$$

If  $B_1 = 1$  then  $A_1 = Q$ , Terminate

$$B_2 = B_1 * F_2$$

If  $B_2 = 1$  then  $A_2 = Q$ , Terminate

$$A_0 = A * F_0$$

$$A_1 = A_0 * F_1$$

$$A_2 = A_1 * F_2$$



◆ Residue Arithmetic

✦ Concept

✦ Advantages

✦ Disadvantages